



Capacitors and Inductors

Dr. Albert T. L. Lee

Department of Electrical and Electronic Engineering
Faculty of Engineering
The University of Hong Kong

Topics

- Properties of Capacitor
- Series and parallel capacitors
- Properties of inductor
- Series and parallel inductors
- Op amp with capacitor


Capacitors and Inductors

- So far, we have focused only on resistive circuits.
- In this chapter, we will learn two other important passive linear circuit elements: **capacitor** and **inductor**.
- Unlike resistors, capacitors and inductors do *not* dissipate energy. Instead, they **store and release energy**.




Capacitors

- A capacitor stores energy in its electric field.
- Typically, a capacitor is constructed as two conducting plates separated by an insulator as shown on the right.
- When a voltage source v is connected to the capacitor, the source deposits positive charges $+q$ on one plate and negative charge $-q$ on the other plate.
- The amount of charge stored is directly proportional to the voltage v , i.e., $q = Cv$, where the proportional constant C is called the capacitance.
- The unit of capacitance is the farad (F).


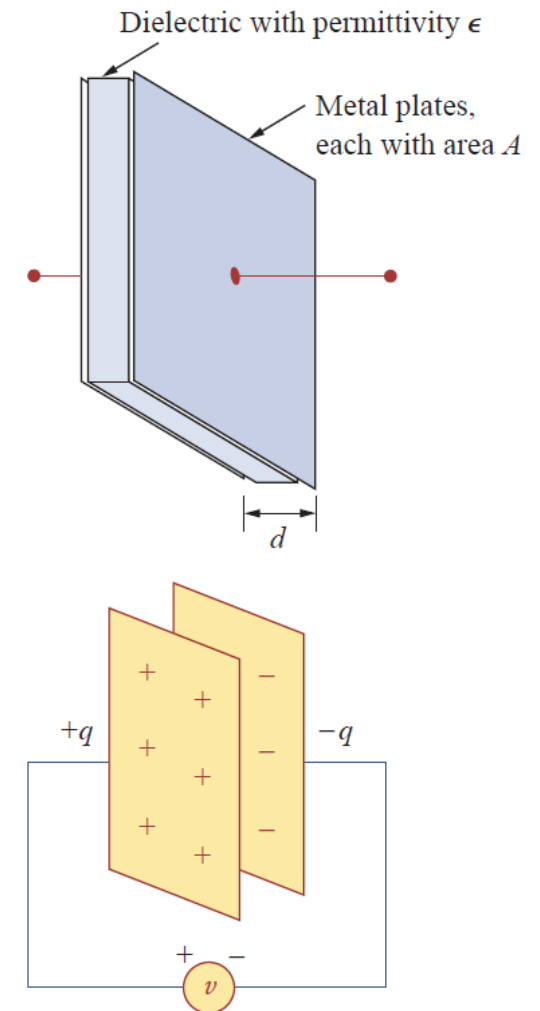


Capacitors (cont'd)

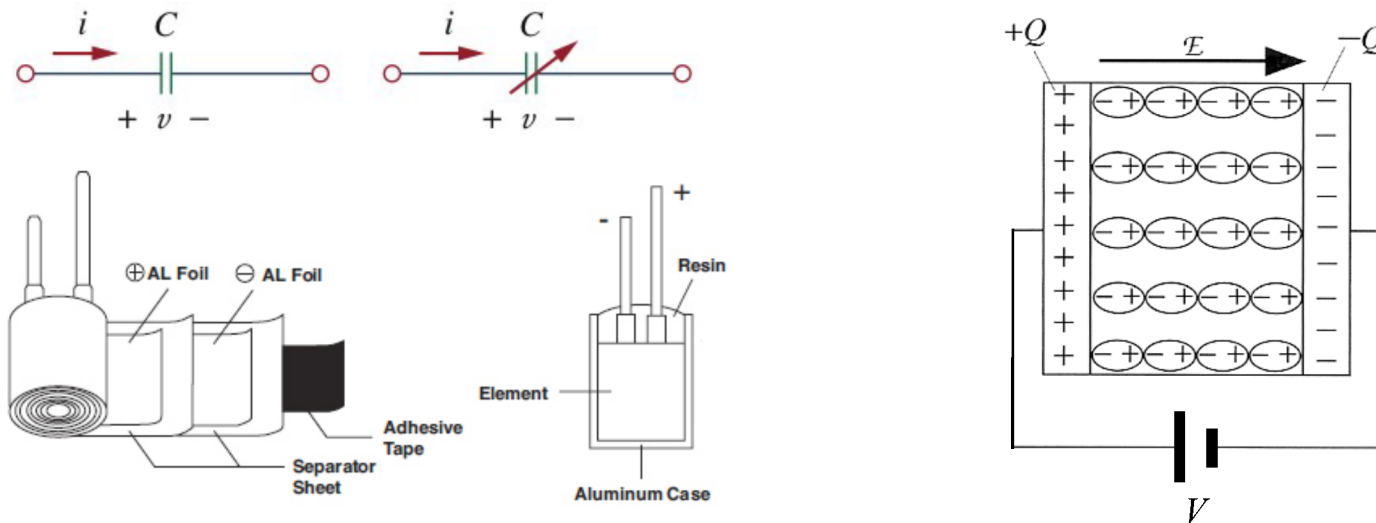- The typical values of commercially-available capacitors are in the range of pF and μF .
- Note that $1 \text{ farad} = 1 \text{ coulomb} / \text{volt}$.
- The symbols of capacitors are shown in the following figure. Note that the current reference direction is going into the positive terminal of the capacitor.



Examples of Capacitor

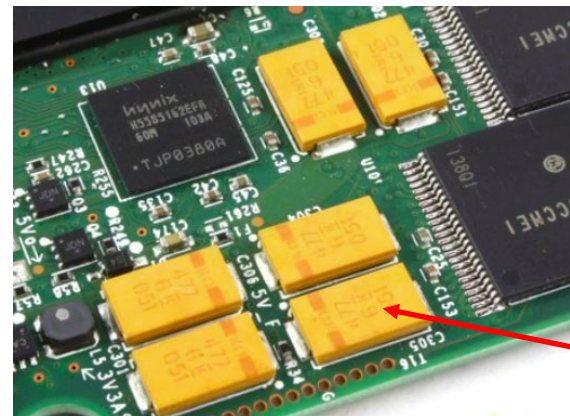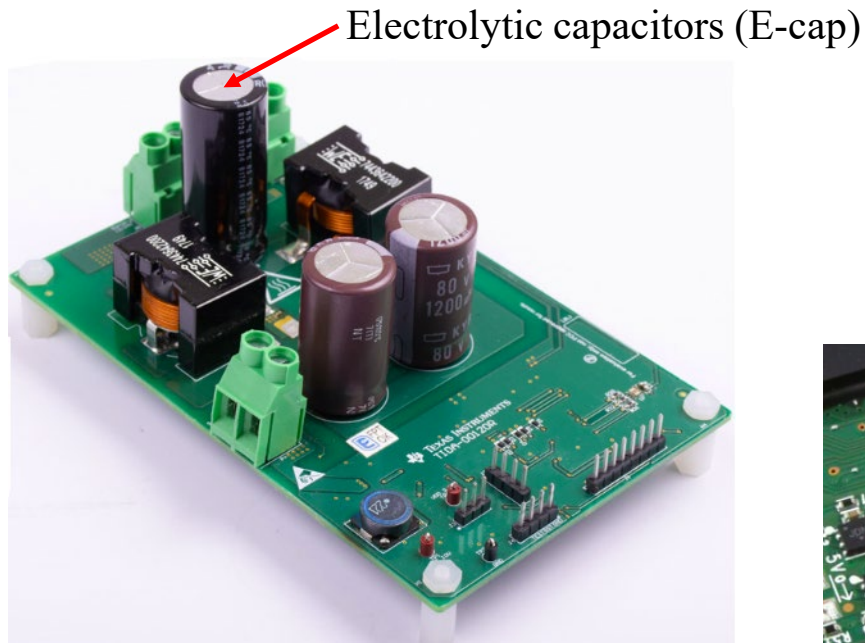

Capacitor Equations

- To obtain the current-voltage relationship, take the derivative on both sides of $q = Cv$ with respect to t . This gives

$$i = C \frac{dv}{dt}$$

- Integrating both sides of the above equation gives the voltage-current relationship.

$$v(t) = \frac{1}{C} \int_{t_o}^t i(t') dt' + v(t_o)$$

- The instantaneous power delivered to the capacitor is: $p = vi = Cv \frac{dv}{dt}$

Capacitor Equations (cont'd)

- The energy stored in the capacitor is therefore given by:

$$w(t) = \int_{-\infty}^t p(t') dt' = C \int_{-\infty}^t v(t') \frac{dv(t')}{dt'} dt' = C \int_{-\infty}^t v dv = \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)}$$

- Assume that the capacitor is uncharged at $t = -\infty$, we have $w(t) = \frac{1}{2} C v(t)^2$

- Key properties of a capacitor:
 - A capacitor is an open circuit to DC after it is fully charged.
 - The voltage on a capacitor cannot change abruptly (a sudden voltage change requires an infinite current).
 - An ideal capacitor does *not* dissipate energy.

Example (1): Capacitors

Question: (a) Calculate the charge stored in a 3 pF capacitor with 20 V across it; and
(b) Find the energy stored in the same capacitor.

Answer: (a) Since $q = Cv$, $q = 3 \times 10^{-12} \times 20 = 60 \text{ pC}$

(b) The energy stored is: $w = \frac{1}{2}Cv^2 = \frac{1}{2}(3 \times 10^{-12})(20)^2 = 6 \times 10^{-10} = 600 \text{ pJ}$

Example (2): Capacitors

Question: The voltage across a $5\text{ }\mu\text{F}$ capacitor is given by $v(t) = 10 \cos(6000t)$.
Calculate the current through it.

Answer: By definition,
$$i(t) = C \frac{dv(t)}{dt} = (5 \times 10^{-6}) \frac{d}{dt} (10 \times \cos 6000t)$$
$$= -5 \times 10^{-6} \times 10 \times 6000 \sin 6000t$$
$$= -0.3 \sin 6000t \text{ A}$$

Example (3): Capacitors

Question: Determine the voltage across a 2 μF capacitor if the current through it is

$i(t) = 6e^{-3000t}$ mA. Assume the capacitor voltage is zero at $t = 0$.

Answer:


- We can use this equation, i.e., $v(t) = \frac{1}{C} \int_{t_o}^t i(t') dt' + v(t_o)$ (1)
- Set $t_o = 0$ and substituting the given expression of $i(t)$ into (1), we have

$$v(t) = \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000t'} dt' \cdot 10^{-3} = \frac{3 \times 10^3}{-3000} e^{-3000t'} \Big|_0^t = (1 - e^{-3000t}) \text{V}$$

Example (4): Capacitors

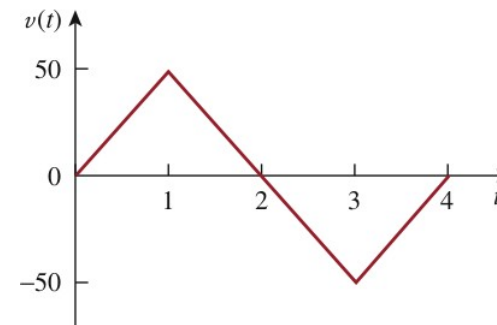Question: Determine the current through a $200\text{ }\mu\text{F}$ capacitor. The voltage across this capacitor can be described mathematically as


$$v(t) = \begin{cases} 50t\text{V} & 0 < t < 1 \\ 100 - 50t\text{V} & 1 < t < 3 \\ -200 + 50t\text{V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$



Answer:

Since $i = Cdv/dt$ and $C = 200\text{ }\mu\text{F}$, we take the derivative of $v(t)$ to obtain $i(t)$ as follows.
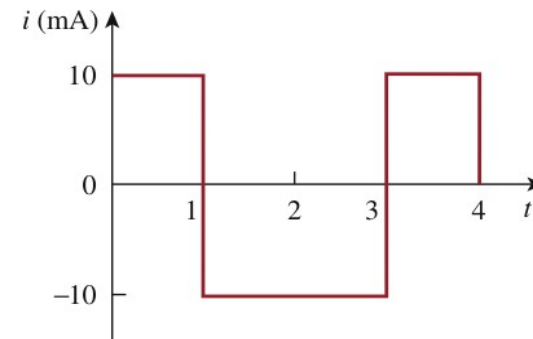
$$i(t) = 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases} = \begin{cases} 10\text{mA} & 0 < t < 1 \\ -10\text{mA} & 1 < t < 3 \\ 10\text{mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$



Example (5): Capacitors

Question: Obtain the energy stored in each capacitor in Fig. (a) under DC conditions.

- Under DC conditions, we replace each capacitor with an open circuit, as shown in Fig. (b).

- The current through the series combination of the $2\text{ k}\Omega$ and $4\text{ k}\Omega$ resistors is obtained by current division as

$$i = \frac{3}{3+2+4}(6\text{mA}) = 2\text{mA}$$



- The voltages v_1 and v_2 across the capacitors can be written as

$$v_1 = 2000i = 4\text{V}, \quad v_2 = 4000i = 8\text{V}$$

- The energies stored in the capacitors can be obtained as

$$w_1 = \frac{1}{2}C_1v_1^2 = \frac{1}{2}(2 \times 10^{-3})(4)^2 = 16\text{mJ}$$
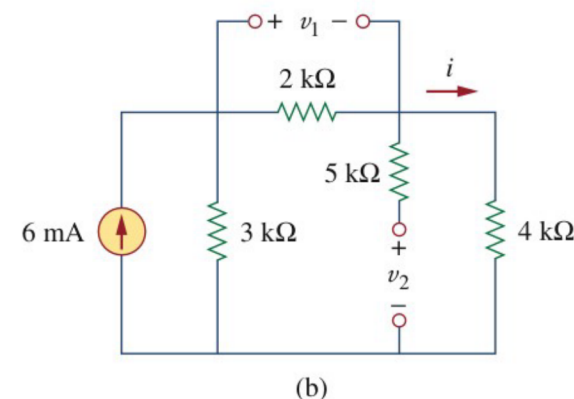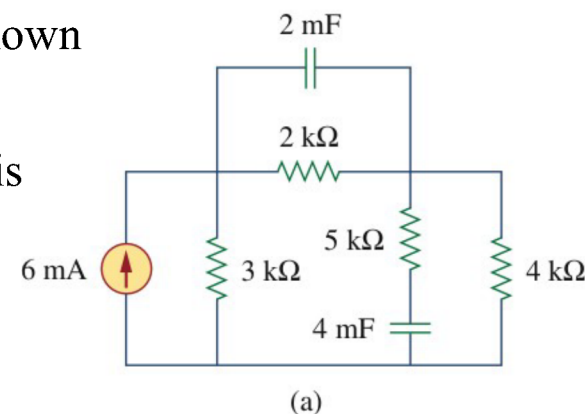
$$w_2 = \frac{1}{2}C_2v_2^2 = \frac{1}{2}(4 \times 10^{-3})(8)^2 = 128\text{mJ}$$




Parallel-connected Capacitors

- We know from resistive circuits that the series-parallel combination is a powerful tool for reducing circuits.
- This technique can be extended to series-parallel connections of capacitors.
- Firstly, consider the case of N capacitors connected in parallel.
 - Since the capacitors have the same voltage v across them, KCL is applied to obtain the total current i , where $i = i_1 + i_2 + \dots + i_N$. But, since $i_k = C_k dv/dt$, we have

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt} = \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$

- Hence, the equivalent capacitance of N parallel capacitors is the sum of the individual capacitances, i.e.,

$$C_{eq} = C_1 + C_2 + \dots + C_N$$

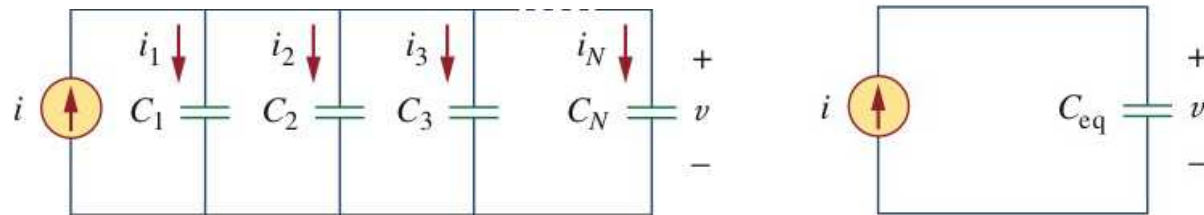

Series-connected Capacitors

- Consider N capacitors connected in series.


- Apply KCL to the loop in Fig. (a), we have

$$v = v_1 + v_2 + \dots + v_N$$

- Notice that the same current i flows through all the capacitors and

$$v_k = \frac{1}{C_k} \int_{t_o}^t i(t) dt + v_k(t_o)$$

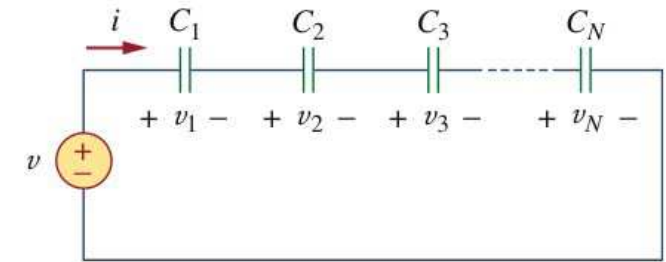- Therefore,
$$v = \frac{1}{C_1} \int_{t_o}^t i(t) dt + v_1(t_o) + \frac{1}{C_2} \int_{t_o}^t i(t) dt + v_2(t_o) + \dots + \frac{1}{C_N} \int_{t_o}^t i(t) dt + v_N(t_o)$$
$$= \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_o}^t i(t) dt + [v_1(t_o) + v_2(t_o) + \dots + v_N(t_o)]$$
$$\triangleq \frac{1}{C_{eq}} \int_{t_o}^t i(t) dt + v(t_o)$$





(a)

Series-connected Capacitors (cont'd)

- From the equation in the previous slide, we know that the equivalent capacitance of series-connected capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

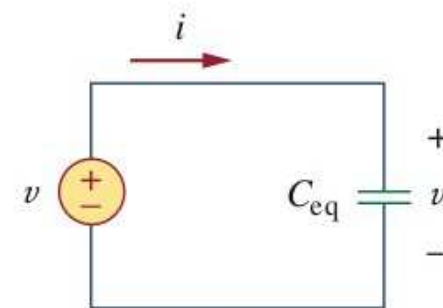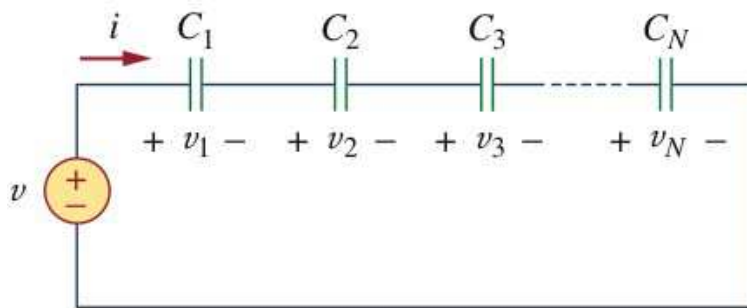In particular, when $N = 2$ (i.e., two capacitors in series), $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$.



Example (6): Capacitors

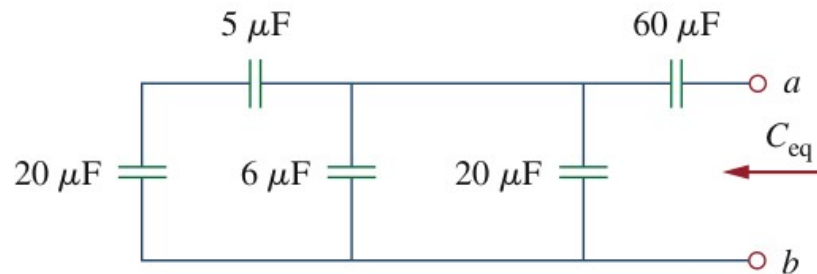Question: Find the equivalent capacitance between terminals a and b in the following circuit.



- The 20 μF and 5 μF capacitors are in series. So, the equivalent capacitance is: $\frac{20 \times 5}{20 + 5} = 4 \mu\text{F}$
- The 4 μF capacitor is in parallel with the 6 μF and 20 μF capacitors. Hence, their combined capacitance is:
 $4 + 6 + 20 = 30 \mu\text{F}$
- The 30 μF capacitor is in series with the 60 μF capacitor. Hence, the equivalent capacitance between terminals a and b (C_{eq}) is given by:

$$C_{eq} = (30 \times 60) / (30 + 60) = 20 \mu\text{F}$$

Inductors


- An inductor stores energy in its magnetic field.

- The voltage-current relationship is given by: $v = L \frac{di}{dt}$

where L is the inductance and the unit is Henry (H).

- Note that the current reference direction is going into the positive side of the voltage polarity.
- The current-voltage relationship is obtained from integrating both sides of above voltage-current relationship, i.e., $di = (1/L)v dt$. Hence, we have
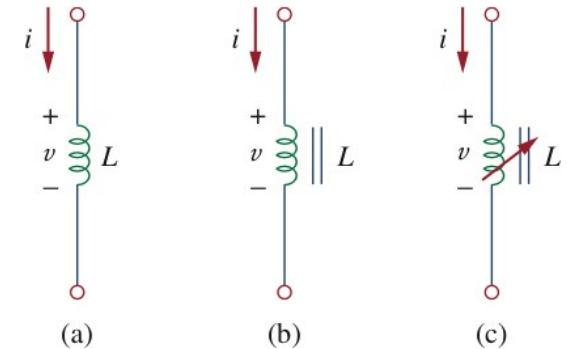
$$i(t) = \frac{1}{L} \int_{t_o}^t v(t') dt' + i(t_o)$$



Inductors (cont'd)


- The power delivered to the inductor is: $p = vi = L(di/dt)i$
- The energy stored is:

$$w(t) = \int_{-\infty}^t p(t')dt' = \int_{-\infty}^t (L \frac{di(t')}{dt'})i(t')dt' = L \int_{-\infty}^t i(t')di(t') = \frac{1}{2}Li^2(t) - \frac{1}{2}Li^2(-\infty)$$

- If we assume $i(-\infty) = 0$, then $w(t) = \frac{1}{2}Li^2(t)$

- Key properties of inductor:

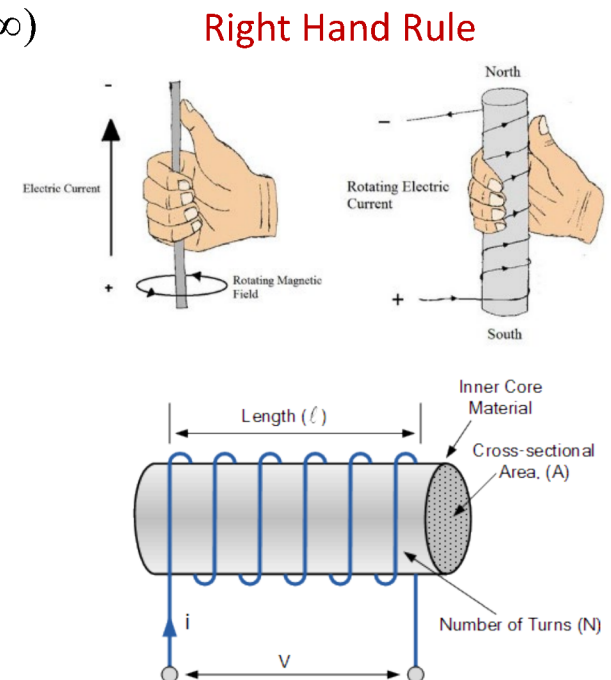- An inductor acts like a short circuit to DC.
- The current through an inductor cannot change instantaneously.
- Ideal inductor does not dissipate energy.



Example (7): Inductors

Question: The current through a 0.1 H inductor is $i(t) = 10te^{-5t}$ A. Determine the voltage across the inductor and the energy stored in it.

- Since $v = Ldi/dt$ and $L = 0.1$ H, $v = 0.1 \frac{d}{dt}(10te^{-5t}) = e^{-5t} + t(-5)e^{-5t} = e^{-5t}(1 - 5t)$ V
- The energy stored is:

$$w(t) = \frac{1}{2}Li(t)^2 = \frac{1}{2}(0.1)100t^2e^{-10t} = 5t^2e^{-10t} \text{ J}$$



Example (8): RLC circuit

Question: In the circuit shown in Fig. (a), assume DC condition, find (a) i , v_c , and I_L ; (b) the energy stored in the capacitor and inductor.

- Under DC condition, the capacitor acts like an open circuit whereas the inductor acts like a short circuit, as shown in Fig. (b).
- (a) From Fig. (b), it is evident that $i = i_L = 12 / (1+5) = 2$ A
The voltage $v_c = 5i_L = 10$ V
- (b) Let w_c and w_L be the energy stored in the capacitor and the inductor, respectively.

$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} (1) (10)^2 = 50 \text{ J}$$
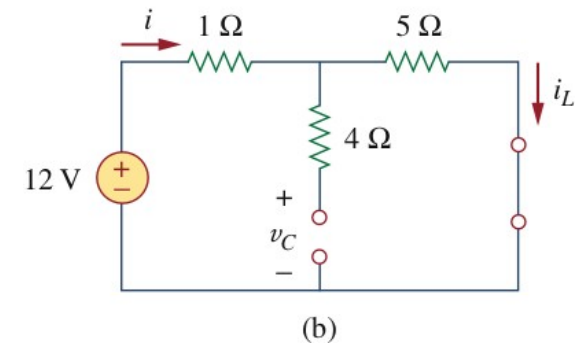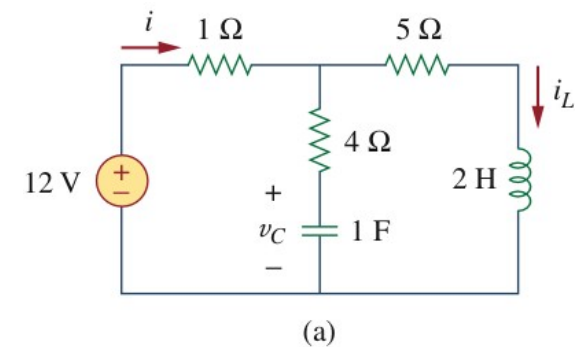
$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (2) (2)^2 = 4 \text{ J}$$




Series-connected Inductors


- Consider a series connection of N inductors, as depicted in Fig. (a).
- The same current (i) flows through all inductors.
- Apply KVL to the loop, $v = v_1 + v_2 + \dots + v_N$.
- Substituting $v_k = L_k di/dt$ yields the following expression.

$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt} = (L_1 + L_2 + \dots + L_N) \frac{di}{dt}$$

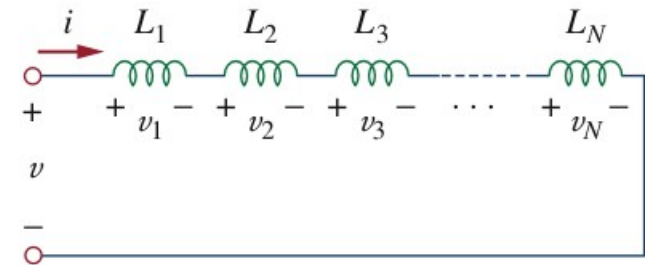- Therefore, $L_{eq} = L_1 + L_2 + \dots + L_N$



(a)

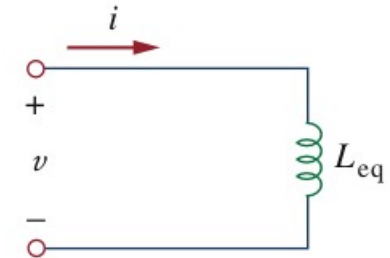

(b)

Parallel-connected Inductors


- Consider N inductors connected in parallel, as depicted in Fig. (a).
- The same voltage (v) is applied across each of the N inductors.
- By applying KCL, $i = i_1 + i_2 + \dots + i_N$.

- Since $i_k = \frac{1}{L_k} \int_{t_o}^t v dt + i_k(t_o)$, we have


$$i = \frac{1}{L_1} \int_{t_o}^t v dt + i_1(t_o) + \frac{1}{L_2} \int_{t_o}^t v dt + i_2(t_o) + \dots + \frac{1}{L_N} \int_{t_o}^t v dt + i_N(t_o)$$
$$= \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_o}^t v dt + \left(\sum_{k=1}^N i_k(t_o) \right)$$

- Therefore, $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$

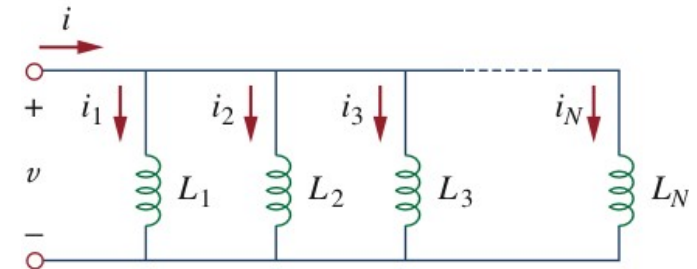- In particular, when $N = 2$, $L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$



(a)

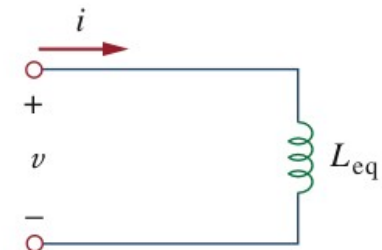


(b)

Summary

Relation	Resistor (R)	Capacitor (C)	Inductor (L)
v - i :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$	$v = L \frac{di}{dt}$
i - v :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
Parallel:	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

Example (9): Inductors

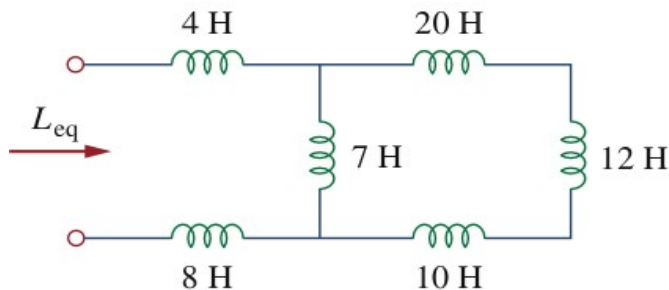
Question: Find the equivalent inductance of the following circuit.



- The 20 H, 12 H and 10 H inductors are connected in series. Thus, their equivalent inductance is 42 H.
- The 42 H inductor is now in parallel with the 7 H inductor. Therefore, they can be combined to give $(42)(7) / (42 + 7) = 6$ H.
- Since the 6 H inductor is in series with the 4 H and 8 H inductors, the equivalent inductance (L_{eq}) is given by the sum of these three inductances, i.e., $L_{eq} = 4 + 6 + 8 = 18$ H.

Example (10): Inductors

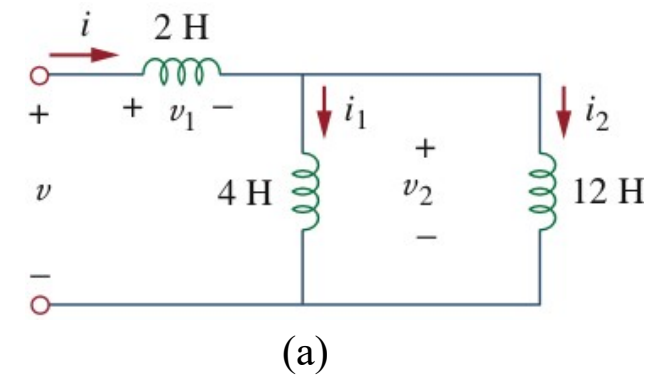Question: Consider the circuit shown in Fig. (a). Given $i(t) = 4(2 - e^{-10t})$ mA. If $i_2(0) = -1$ mA, find (a) $i_1(0)$; (b) $v(t)$, $v_1(t)$, and $v_2(t)$; (c) $i_1(t)$ and $i_2(t)$.



- (a) From $i(t) = 4(2 - e^{-10t})$, $i(0) = 4(2 - 1) = 4$ mA. Since $i = i_1 + i_2$, $i_1(0) = i(0) - i_2(0) = 4 - (-1) = 5$ mA.
- (b) $L_{eq} = 2 + (4 \parallel 12) = 2 + 3 = 5$ H.
Thus, $v(t) = L_{eq} di/dt = 5(4)(-1)(-10)e^{-10t} = 200e^{-10t}$ mV
 $v_1(t) = 2 di/dt = 2(4)(-1)(-10)e^{-10t} = 80e^{-10t}$ mV
 $v_2(t) = v(t) - v_1(t) = 120e^{-10t}$ mV
- (c)
$$i_1(t) = \frac{1}{4} \int_0^t v_2(t') dt' + i_1(0) = \frac{120}{4} \int_0^t e^{-10t'} dt' + 5 \text{ mA} = -3e^{-10t'} \Big|_0^t + 5 \text{ mA} = 8 - 3e^{-10t} \text{ mA}$$
$$i_2(t) = \frac{1}{12} \int_0^t v_2(t') dt' + i_2(0) = \frac{120}{12} \int_0^t e^{-10t'} dt' - 1 \text{ mA} = -e^{-10t'} \Big|_0^t - 1 \text{ mA} = -e^{-10t} \text{ mA}$$

Op Amp with Capacitor

- By replacing the feedback resistor (R_f) in the familiar inverting amplifier in Fig. (a) with a capacitor, an integrator can be obtained, as shown in Fig. (b).

- At node a in Fig. (b), we have $i_R = i_C$.

- But, $i_R = v_i / R$ and $i_C = -C dv_o / dt$

- By equating i_R and i_C , we have



$$\frac{v_i}{R} = -C \frac{dv_o}{dt} \Rightarrow dv_o = -\frac{1}{RC} v_i dt$$

- By integrating both sides of the above equation gives:

$$v_o(t) - v_o(0) = -\frac{1}{RC} \int_0^t v_i(t') dt'$$

- If the capacitor is not charged at $t = 0$, we have
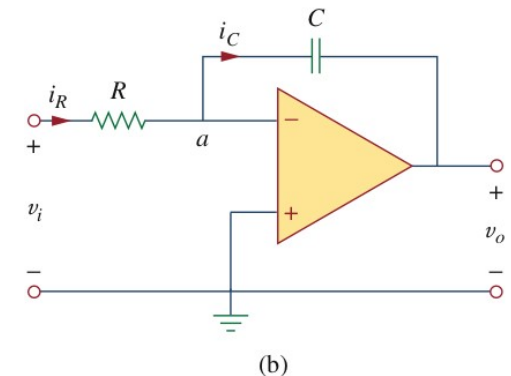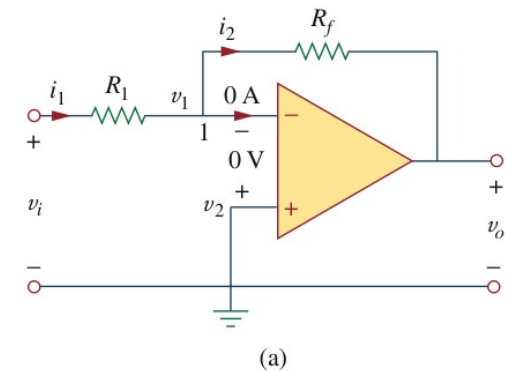
$$v_o(t) = -\frac{1}{RC} \int_0^t v_i(t') dt'$$




Example (11): Op Amp with Capacitor

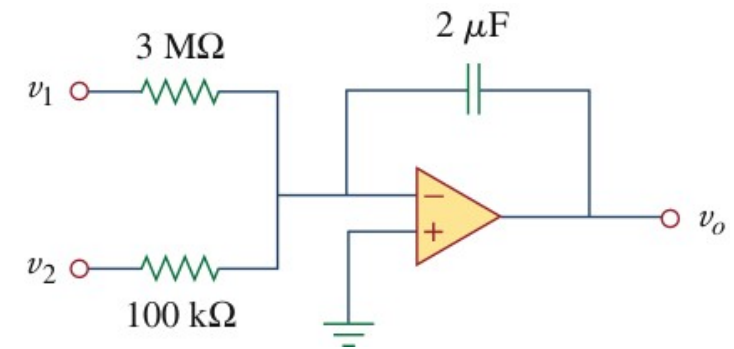Question: If $v_1(t) = 10 \cos 2t$ mV and $v_2(t) = 0.5t$ mV, find $v_o(t)$ in the following op amp circuit. Assume the voltage across the capacitor is initially zero.

This is a summing integrator whose output voltage can be expressed as

$$\begin{aligned} v_o &= -\frac{1}{R_1 C} \int_0^t v_1(t') dt' - \frac{1}{R_2 C} \int_0^t v_2(t') dt' \\ &= -\frac{1}{3 \times 10^6 \times 2 \times 10^{-6}} \int_0^t 10 \cos 2t' dt' - \frac{1}{100 \times 10^3 \times 2 \times 10^{-6}} \int_0^t 0.5t' dt' \\ &= -\frac{1}{6} \frac{10}{2} \sin 2t - \frac{1}{0.2} \frac{0.5t^2}{2} \\ &= -0.833 \sin 2t - 1.25t^2 \text{ mV} \end{aligned}$$




Differentiator

- If the input resistor in the inverting amplifier is replaced by a capacitor, as shown in the following op amp circuit, we have a differentiator.

- Apply KCL at node a , we have $i_C = i_R$.
- But, $i_C = Cdv_i/dt$ and $i_R = -v_o / R$
- By equating i_C and i_R , we have

$$v_o = -RC \frac{dv_i}{dt}$$

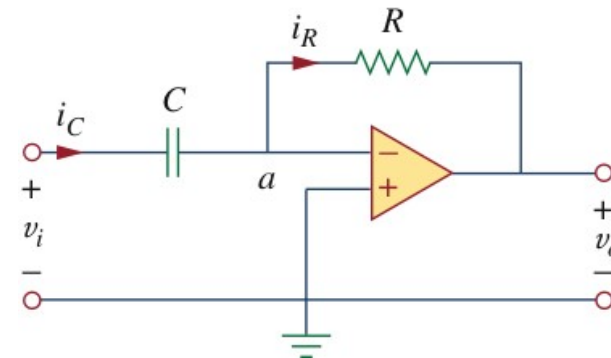

- Although inductors can theoretically be used with op amp, they are seldom used in practice because they tend to be more bulky and expensive.

Example (12): Op Amp with Capacitor



Question: Sketch the output voltage (v_o) for the circuit in Fig. (a), given the input voltage in Fig. (b). Assume $v_o = 0$ at $t = 0$.

- Observe that this is a differentiator with $RC = 5 \times 10^3 \times 0.2 \times 10^{-6} = 10^{-3}$ s.
- From Fig. (b), for $0 < t < 4$ ms, the input voltage (v_i) can be expressed as

$$v_i = \begin{cases} 2000t & 0 < t < 2 \text{ ms} \\ 8 - 2000t & 2 < t < 4 \text{ ms} \end{cases}$$

- The output voltage can be obtained as


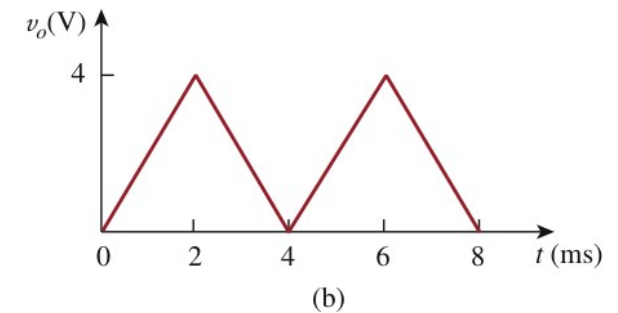
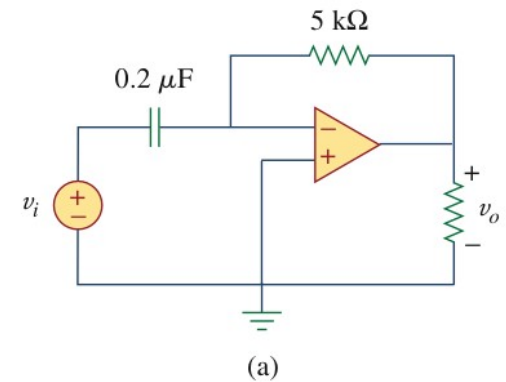
$$v_o = -RC \frac{dv_i}{dt} = \begin{cases} -2\text{V} & 0 < t < 2 \text{ ms} \\ 2\text{V} & 2 < t < 4 \text{ ms} \end{cases}$$



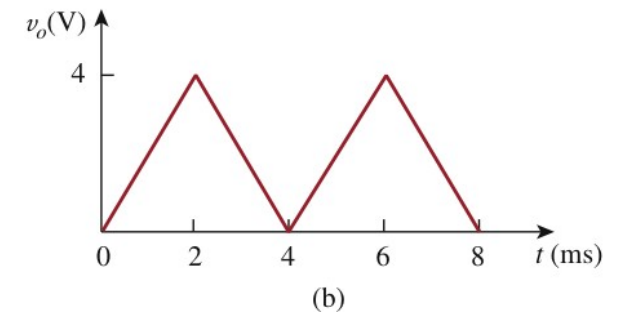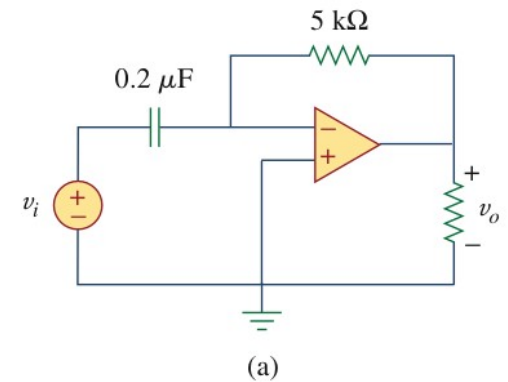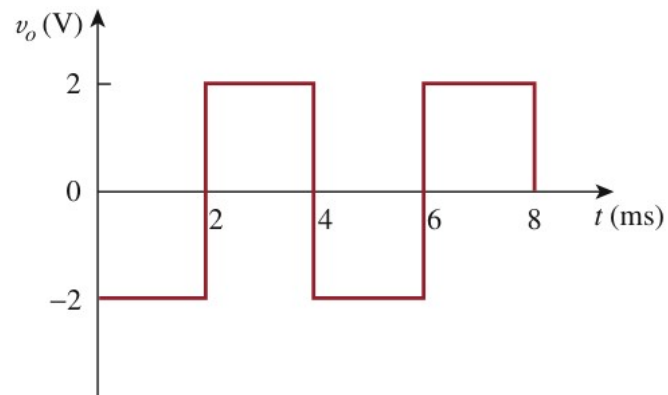Example (12): Op Amp with Capacitor

(Cont'd)

- From Fig. (b), for $4 < t < 8$ ms, the output voltage (v_o) is the same as that for $0 < t < 4$ ms.
- Thus, the output voltage is sketched below.



Analog Computer

- Op amps were originally developed for electronic analog computers.
- Analog computers can be programmed to solve mathematical models of mechanical or electrical systems. These models are often expressed in terms of differential equations.
- Solving simple differential equations using the analog computer requires cascading three types of op amp circuits, namely, integrator circuits, summing amplifiers, and inverting (or non-inverting) amplifiers for negative or positive scaling.

Suppose we would like to find the solution $x(t)$ of the following equation.

$$a \frac{d^2x}{dt^2} + b \frac{dx}{dt} + cx = f(t), \quad t > 0$$

where a , b , and c are constants, and $f(t)$ is an arbitrary forcing function.

Analog Computer (cont'd)

$$a \frac{d^2x}{dt^2} + b \frac{dx}{dt} + cx = f(t), \quad t > 0$$

where a, b, and c are constants, and $f(t)$ is an arbitrary forcing function.

The solution can be obtained by first solving the highest-order derivative term. That is,

$$\frac{d^2x}{dt^2} = \frac{f(t)}{a} - \frac{b}{a} \frac{dx}{dt} - \frac{c}{a} x$$

Now, to obtain dx/dt , the d^2x/dt^2 term is integrated.

Likewise, to obtain x , the dx/dt term is integrated.

Hence, the analog computer is implemented by connecting the necessary summers, inverters, and integrators.

Example (13): Analog Computer

Question: Design an analog computer circuit to solve the following differential equation.

$$\frac{d^2 v_o}{dt^2} + 2 \frac{dv_o}{dt} + v_o = 10 \sin 4t, \quad t > 0$$


Subject to $v_o(0) = -4$ and $v_o'(0) = 1$, where the prime refers to the time derivative.

Solution:

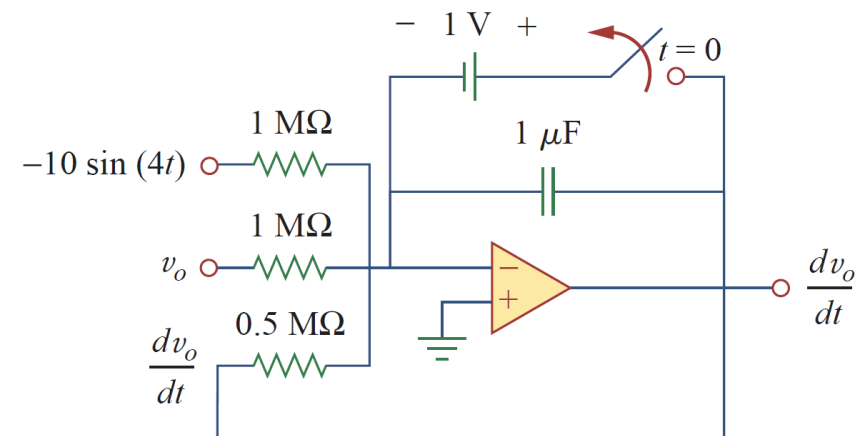1. We implement equation using the **summing integrator**

$$\frac{dv_o}{dt} = - \int_0^t \left(-10 \sin 4t + 2 \frac{dv_o}{dt} + v_o \right) dt + v_o'(0)$$

$$-\frac{1}{RC} \int_0^t v_o dt \quad RC=1$$




Example (13): Analog Computer (cont'd)

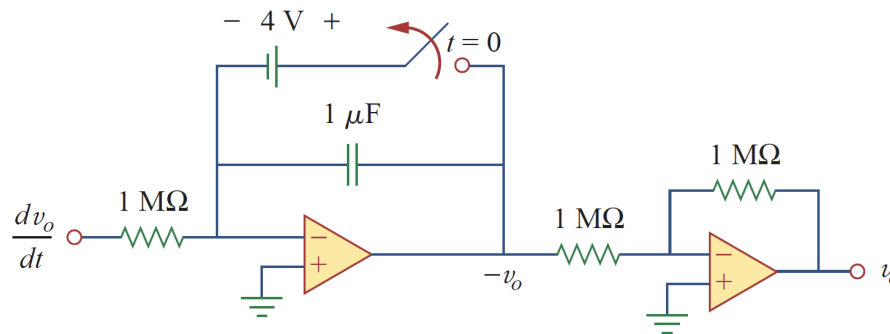2. The next step is to obtain v_o by integrating dv_o/dt and inverting the result.

$$v_o = - \int_0^t \left(- \frac{dv_o}{dt} \right) dt + v(0)$$

$$- \frac{1}{RC} \int_0^t v_o dt \quad RC=1$$



Example (13): Analog Computer (cont'd)

$$\frac{d^2 v_o}{dt^2} + 2 \frac{dv_o}{dt} + v_o = 10 \sin 4t, \quad t > 0$$

