



# Basic Circuit Principles

Dr. Albert T. L. Lee

Department of Electrical and Electronic Engineering  
Faculty of Engineering  
The University of Hong Kong



# Basic Concepts

I. Charge and Current

II. Voltage

III. Power and Energy

IV. Circuit Element

# Motivation



- An electric circuit is an interconnection of electrical elements.
- What is circuit analysis ?

To predict how a circuit behaves without implementing it

- For a simple circuit, it is trivial

$$I = 10 \text{ V} / 5 \Omega = 2 \text{ A}$$

- How about this ?

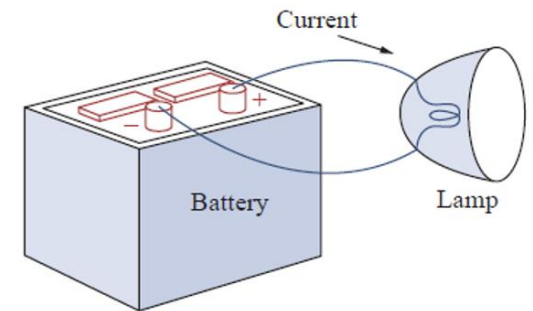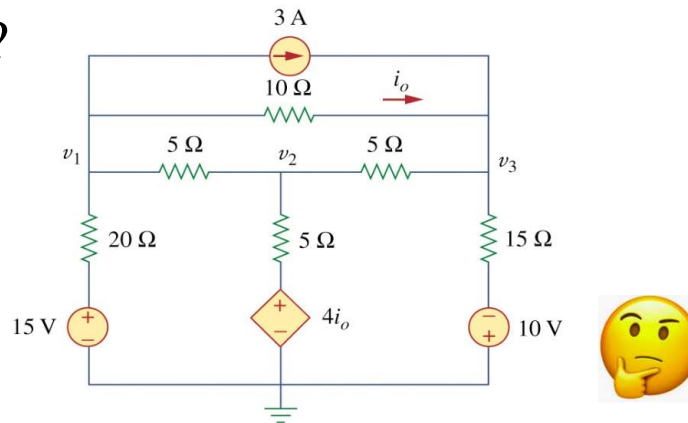

# International Systems of Units (SI)

- Universal language of measurement
- The metric system is often referred to as the SI unit which is based on the number 10 and multiples of 10.

Example: 100,000,000 mm    100,000 m    100 km

Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd
Amount of substance	mole	mol

Multiplier	Prefix	Symbol
$10^{18}$	exa	E
$10^{15}$	peta	P
$10^{12}$	tera	T
$10^9$	giga	G
$10^6$	mega	M
$10^3$	kilo	k
$10^2$	hecto	h
10	deka	da
$10^{-1}$	deci	d
$10^{-2}$	centi	c
$10^{-3}$	milli	m
$10^{-6}$	micro	$\mu$
$10^{-9}$	nano	n
$10^{-12}$	pico	p
$10^{-15}$	femto	f
$10^{-18}$	atto	a



**I. Charge and Current**

II. Voltage

III. Power and Energy


IV. Circuit Element

# Charge and Current

- Electrons have a negative charge (Q) measured in coulombs (C).
  - charge on a proton is  $+1.602 \times 10^{-19} \text{ C}$
  - charge on an electron is  $-1.602 \times 10^{-19} \text{ C}$

What is current?

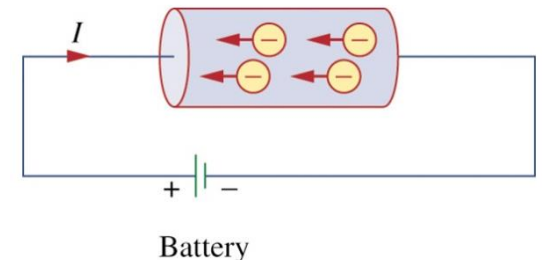- Net movement of electrons carrying negative charges.
- By convention, the **direction of electric current** is the direction in which a positive charge would move from positive to negative charged terminal in a closed circuit.
- Current and electrons move in opposite directions.



# Charge and Current

- Electric current is the amount of charge flowing per second (rate of change of charge) and is given the unit ampere (A).
- Mathematically, it is given by

$$i(t) = \frac{dq(t)}{dt}$$

Diagram illustrating the components of the current equation  $i(t) = \frac{dq(t)}{dt}$ :

- $i(t)$  is labeled as Current in amperes (A).
- $dq(t)$  is labeled as Charge transferred in coulombs (C).
- $dt$  is labeled as Time duration in seconds (s).

- A current of 1 A means 1 C of charge moving across a fixed surface in 1 s.
- The charge transferred between time  $t_0$  and  $t_1$  is given by the inverse relationship:

$$Q = \int_{t_0}^{t_1} i(t) dt$$

# Example (1)

(1) The total charge entering a terminal is given by:

$$q(t) = 5t \sin(4\pi t) \text{ mC}$$

Calculate the current at  $t = 0.5$  s.

*By applying the Product Rule, we have*

$$\frac{d}{dx}(u \cdot v) = u \cdot \frac{dv}{dx} + v \cdot \frac{du}{dx}$$

Ans:

$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt} [5t \sin(4\pi t)] = 5 \sin(4\pi t) + 20\pi t \cos(4\pi t)$$

$$i(0.5) = 5 \sin(2\pi) + 10\pi \cos(2\pi) \approx 31.42 \text{ mA}$$



## Example (2)

(1) The charge profile entering a certain element across time is shown in Fig. 1. Find the current at (a)  $t = 1$  ms, (b)  $t = 6$  ms, and (c)  $t = 10$  ms.

(Hint: Current is the *slope* of the curve.)

Ans: (a)  $i(1 \text{ ms}) = 80/2 = 40 \text{ A}$

(b)  $i(6 \text{ ms}) = 0 \text{ A}$

(c)  $i(10 \text{ ms}) = -80/4 = -20 \text{ A}$

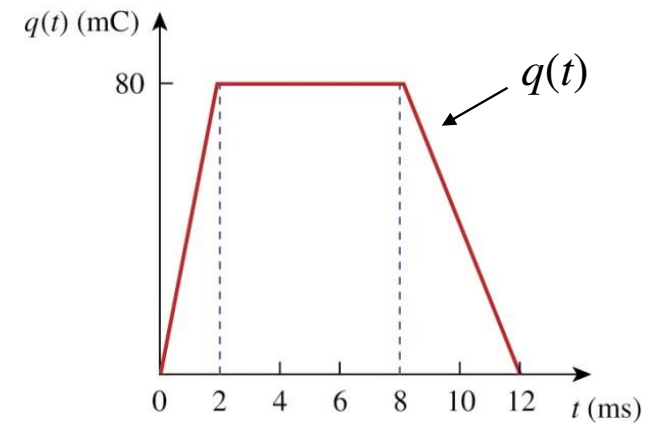


Fig. 1

(2) Determine the total charge entering a terminal between  $t = 1$  s and  $t = 2$  s if the current across the terminal is given by:  $i(t) = (6t^2 - t) \text{ A}$ .

$$\text{Ans: } Q = \int_1^2 i(t) dt = \int_1^2 (6t^2 - t) dt = \left( 2t^3 - \frac{t^2}{2} \right) \bigg|_1^2 = (16 - 2) - \left( 2 - \frac{1}{2} \right) = 12.5 \text{ C}$$



I. Charge and Current

**II. Voltage**

III. Power and Energy

IV. Circuit Element

# Voltage

- Electric current does not flow on its own (free electrons in conductors are in random motions with zero net flow).
- To move an electron from point  $a$  to point  $b$ , an external electromotive force (EMF), e.g. battery, is needed.
- The strength of the EMF is expressed in **voltage** and is measured in **volts (V)**.
- The voltage  $v_{ab}$  between two points  $a$  and  $b$  is the energy required to move a unit charge from  $a$  to  $b$ . Mathematically,


$$v_{ab} = \frac{dw}{dq}$$

Diagram illustrating the definition of voltage  $v_{ab}$ :

- $v_{ab}$  is labeled as Voltage in volts (V).
- $dw$  is labeled as Energy in joules (J).
- $dq$  is labeled as Charge transferred in coulombs (C).


- 1 volt = 1 joule / coulomb ( $1 \text{ V} = 1 \text{ J C}^{-1}$ ).

# Voltage

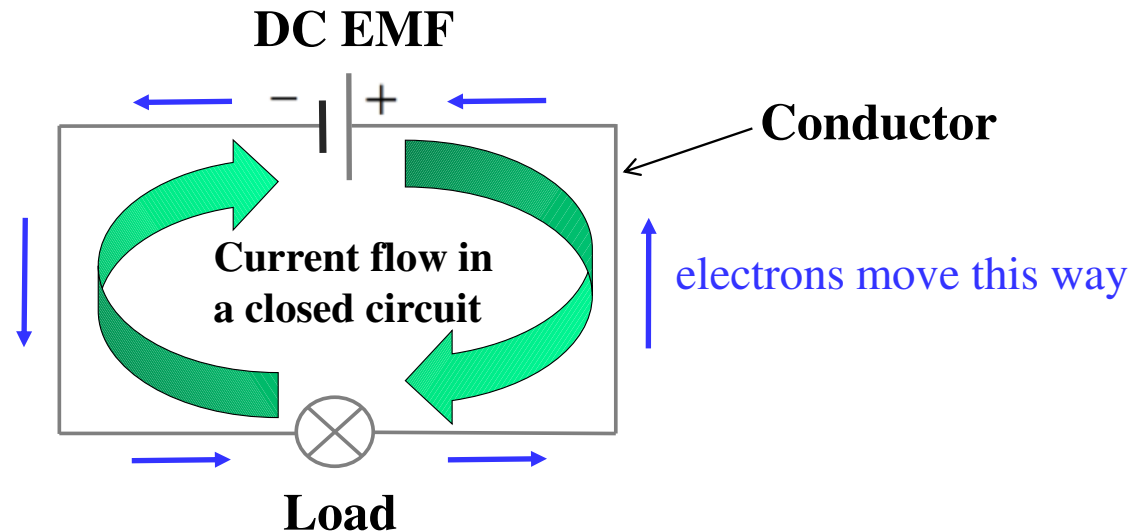

- If the voltage of the DC EMF is maintained between two points of a circuit, ***current will flow in one direction*** – from high (+) to low (–) potential.
- This is called a ***direct current (DC) circuit***.
- Battery-powered circuits are DC circuits.

# Voltage

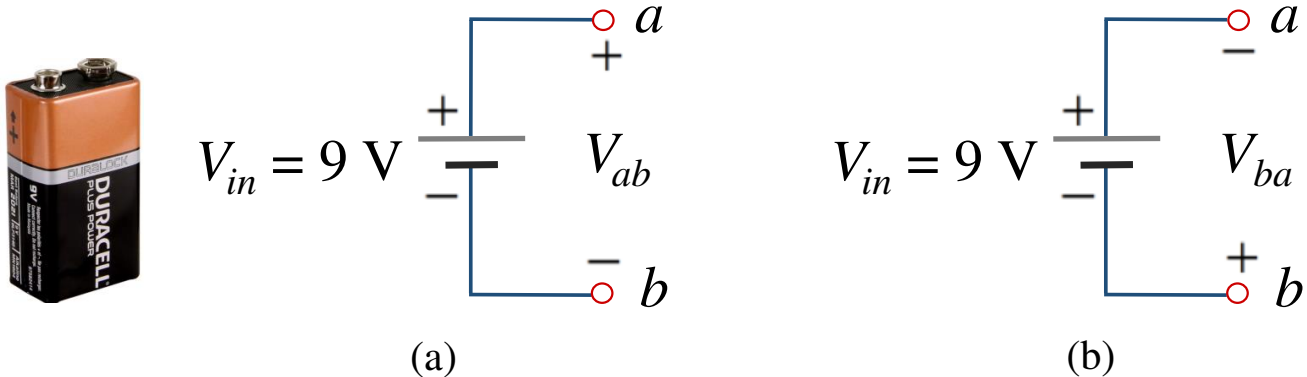

Without loss of generality, assume point  $b$  is connected to ground. So,  $V_b = 0\text{ V}$ .

Case (a):  $V_{in} = V_{ab} = V_a - V_b = 9\text{ V} - 0\text{ V} = +9\text{ V}$

Case (b):  $V_{in} = -V_{ba} = -(V_b - V_a) = -(0\text{ V} - 9\text{ V}) = +9\text{ V}$

Hence, case (a) and (b) are equivalent, i.e.,  $V_{ab} = -V_{ba}$ .

Voltage (or potential difference), measured in volts (V), is defined as the energy required to move a unit charge through an element.



I. Charge and Current

II. Voltage

**III. Power and Energy**


IV. Circuit Element

# Power and Energy

- Power is the rate (w.r.t. time) of expending or absorbing energy, measured in **watts (W)**.
- Mathematically,


$$p(t) = \frac{dw(t)}{dt} \Rightarrow p(t) = \frac{dw(t)}{dq(t)} \frac{dq(t)}{dt} = v(t)i(t)$$

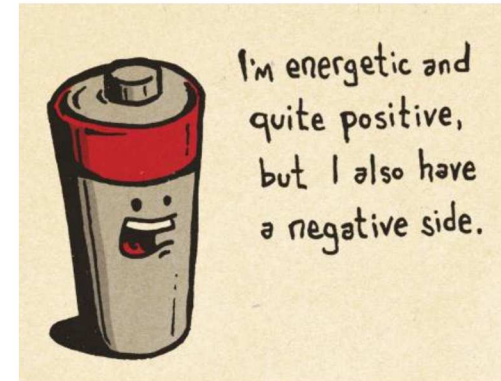- The sign of power across a circuit element depends on the current direction and voltage difference across that element.
- In DC circuits, since  $p(t)$ ,  $v(t)$  and  $i(t)$  are constants,  $p(t) = P = VI$ .



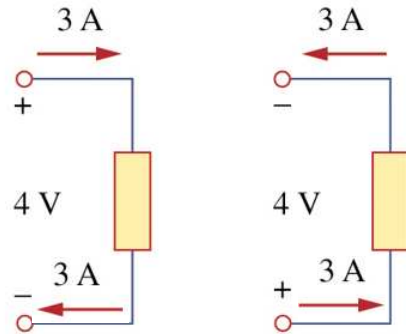
# Power and Energy

- The element absorbs (consumes) a power of +12 W.



The 3 A current flows into the **positive** terminal of the element, i.e., it goes from a higher potential to lower potential.

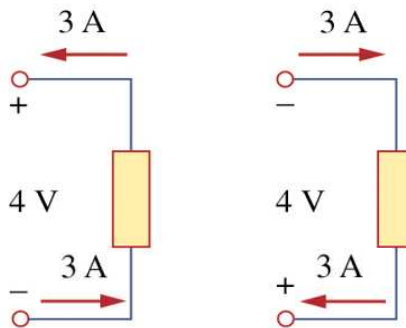
- The element absorbs a power of  $-12$  W (or supplies a power of +12 W).



The 3 A current flows into the **negative** terminal of the element, i.e., it goes from a lower potential to a higher potential.



# Power and Energy

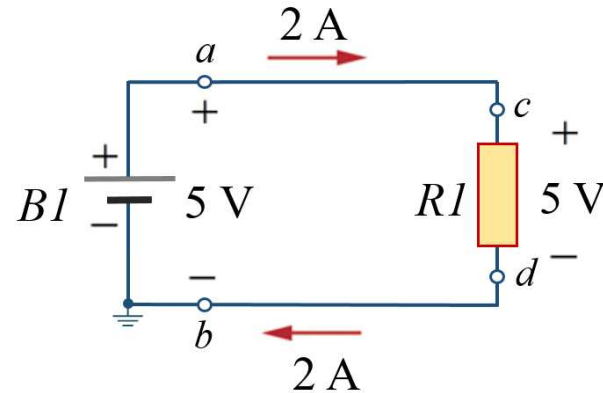

- Based on the current direction, the voltage across the battery  $B1$  (i.e., from point  $b$  to point  $a$ ):  
 $V_{ba} = V_b - V_a = 0\text{ V} - 5\text{ V} = -5\text{ V}$
- Likewise, the voltage across the load  $R1$  (i.e., from point  $c$  to point  $d$ ):  
 $V_{cd} = V_c - V_d = 5\text{ V} - 0\text{ V} = 5\text{ V}$  (Note:  $V_{cd} = -V_{ba} = 5\text{ V}$ )
- Power absorbed by  $B1$ :  $P_{B1} = V_{ba} I = -5\text{ V} \times 2\text{ A} = -10\text{ W}$   
(or equivalently,  $B1$  supplies a power of  $+10\text{ W}$ .)
- Power absorbed by  $R1$ :  $P_{R1} = V_{cd} I = 5\text{ V} \times 2\text{ A} = 10\text{ W}$

# Power and Energy


Recall:  $p(t) = \frac{dw(t)}{dt}$

Energy absorbed (or supplied) by a circuit element from time  $t_0$  to  $t_1$ :

$$w = \int_{t_0}^{t_1} p(t) dt = \int_{t_0}^{t_1} v(t)i(t) dt$$

In particular, when  $p(t)$  is a constant (i.e.,  $p(t) = P_o$ ), we have

$$w = P_o (t_1 - t_0)$$

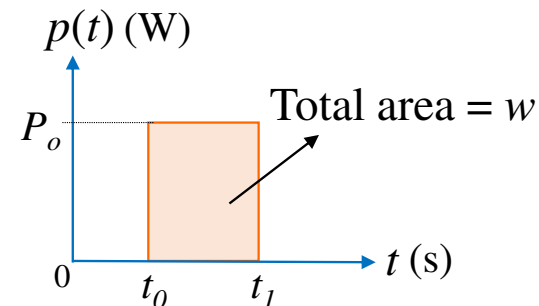

# Example (3)

(1) Find the power delivered to an electronic load at  $t = 10$  ms if the current entering its positive terminal is  $i(t) = 5\cos(2\pi t)$  A and the voltage is: a)  $v = 3i$ ; b)  $v = 3di/dt$ .

Ans: (a)  $p(t) = v(t)i(t) = 3[i(t)]^2 = 75\cos^2 2\pi t$  W

$$\Rightarrow p(0.01) = 75\cos^2(0.02\pi) \approx 74.7 \text{ W}$$

(b)  $v(t) = 3di/dt = -30\pi[\sin(2\pi t)]$

$$\Rightarrow p(t) = v(t)i(t) = -150\pi[\sin(2\pi t)][\cos(2\pi t)] \text{ W}$$

$$\Rightarrow p(0.01) = -150\pi[\sin(0.02\pi)][\cos(0.02\pi)] = -29.53 \text{ W}$$

(2) How much energy does a 100 W LED light bulb consume in two hours ?

Ans: Since  $p$  is a constant (i.e.,  $p(t) = P_{LED} = 100$  W),  $w = P_{LED}t = 100 \times 2 \times 3600 = 720$  kJ



I. Charge and Current


II. Voltage

III. Power and Energy

**IV. Circuit Element**
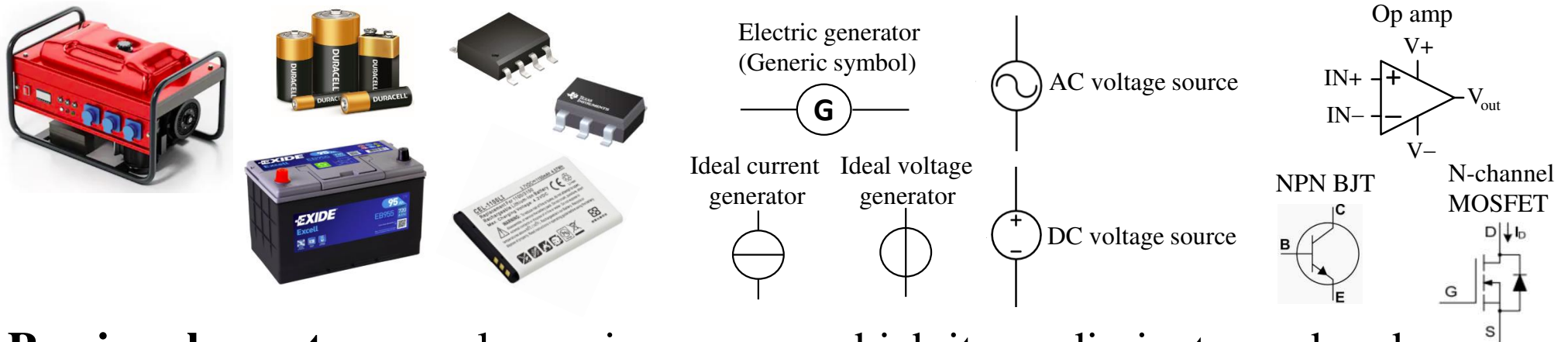
# Circuit Element

- **Active elements** are capable of generating or supplying energy to a circuit.  
e.g. generator, battery, operational amplifier (op amp), and transistors.



- **Passive elements** can only receive energy, which it can dissipate or absorb.  
e.g. resistors, capacitors, and inductors.





# Voltage Source & Current Source

There are two important active elements: (a) voltage source and (b) current source.



Definition:

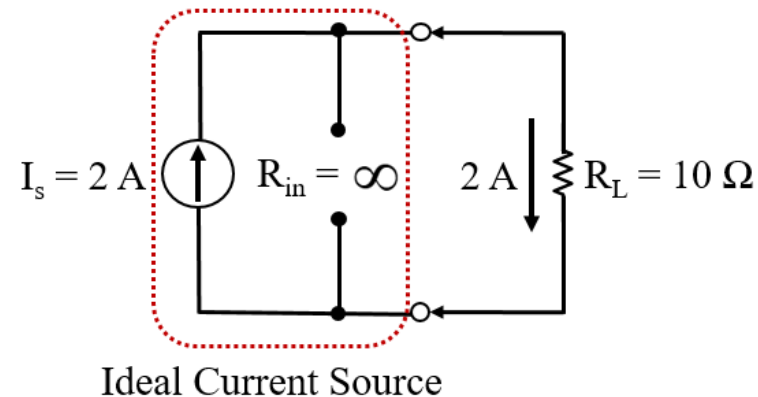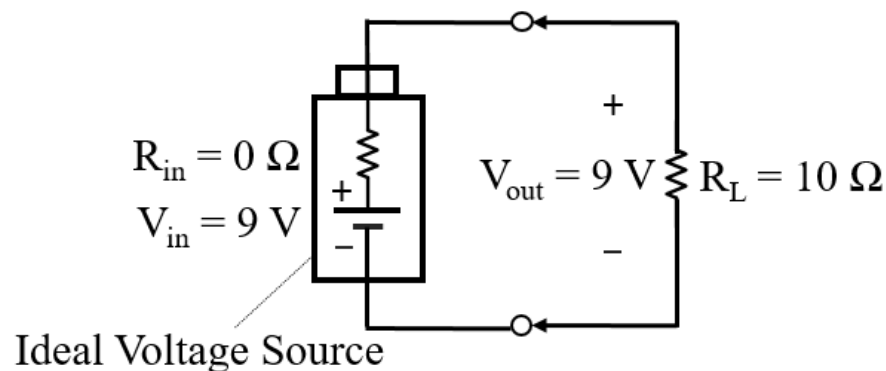- (i) **Ideal voltage source** is a voltage source that supplies constant voltage to a circuit despite the current which the circuit draws. It has zero internal resistance.
- (ii) **Ideal current source** is a current source that supplies constant current to a circuit despite any other conditions present in the circuit. It has infinite internal resistance.



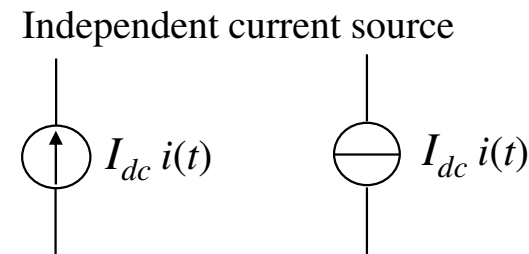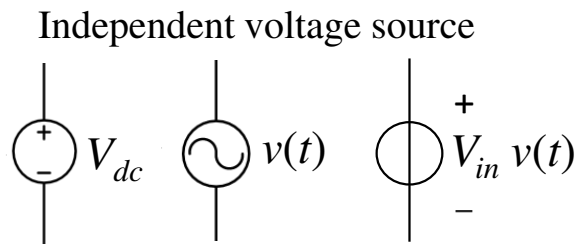
# Independent vs Dependent Source

- Independent voltage (current) source** maintains a specified voltage (current) whose value is *not* affected by other circuit elements.




- Dependent voltage (current) source** has its voltage (current) value varying with another variable (or a set of variables). It is designated by a diamond-shaped symbol.


Voltage controlled voltage source

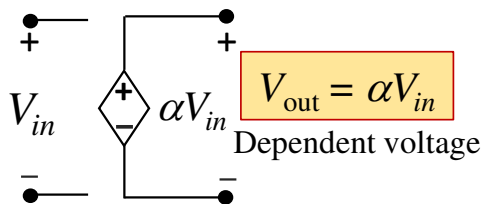


Current controlled voltage source

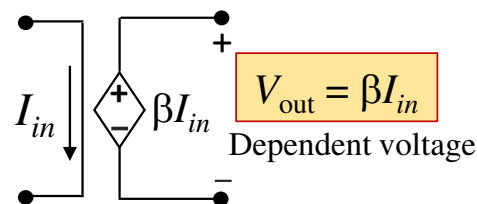

Voltage controlled current source

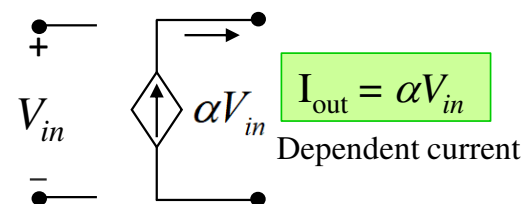


Current controlled current source

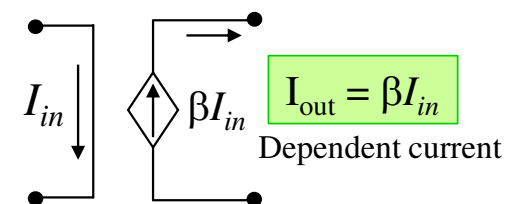

# Example (4)

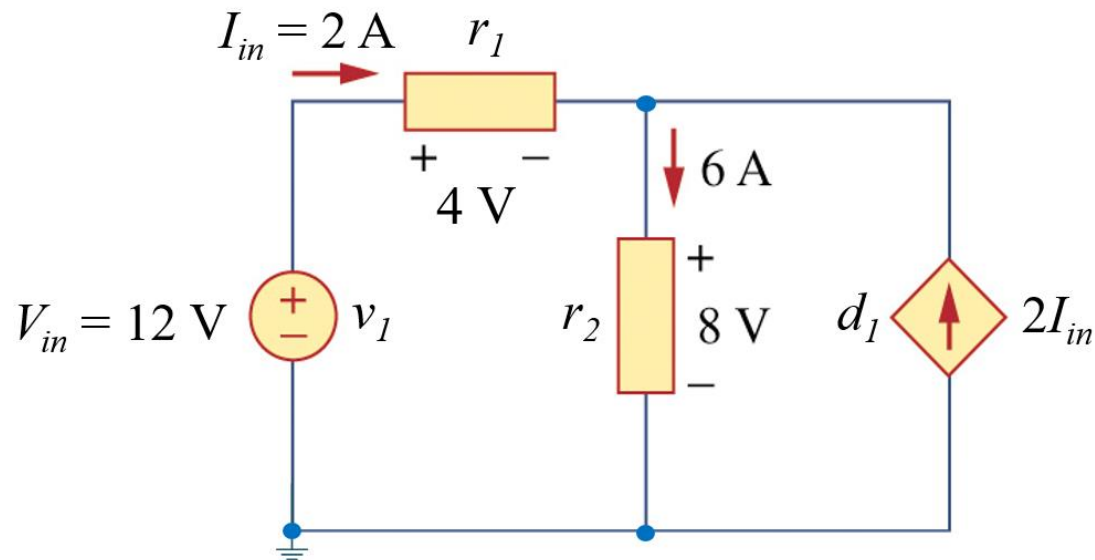- (1) Calculate the power absorbed (dissipated) by each element in the following circuit.




(Hint: Consider the direction of the current across each element.)



# Example (4) cont'd

Ans:

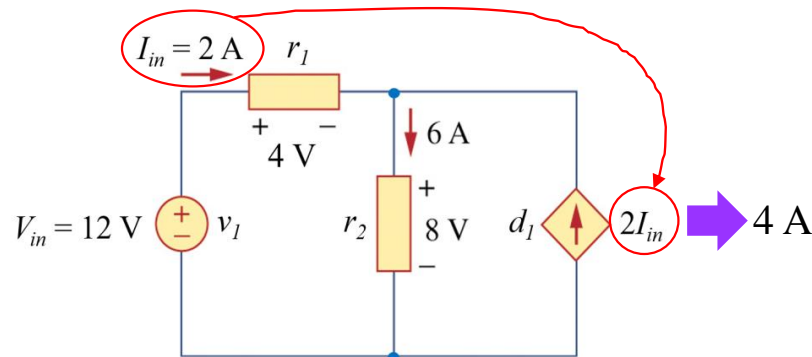


Technique:

First determine the values of the dependent sources wherever possible.

- For  $v_1$ : Since the 2 A current flows out of the positive terminal of  $v_1$ , the power absorbed by  $v_1$  is:  
 $P_{v1} = -V_{in} I_{in} = -12(2) = -24 \text{ W}$  (In other words,  $v_1$  supplies +24 W of power).
- For  $r_1$ : Since the 2 A current flows into the positive terminal of  $r_1$ , the power absorbed by  $r_1$  is:  
 $P_{r1} = V_{r1} I_{r1} = 4(2) = 8 \text{ W}$
- For  $r_2$ : Since the 6 A current flows into the positive terminal of  $r_2$ , the power absorbed by  $r_2$  is:  
 $P_{r2} = V_{r2} I_{r2} = 8(6) = 48 \text{ W}$
- For  $d_1$ : Since the 4 A current flows out of the positive terminal of  $d_1$ , the power absorbed by  $d_1$  is:  
 $P_{d1} = -V_{d1} I_{d1} = -8(4) = -32 \text{ W}$


# Example (4) cont'd

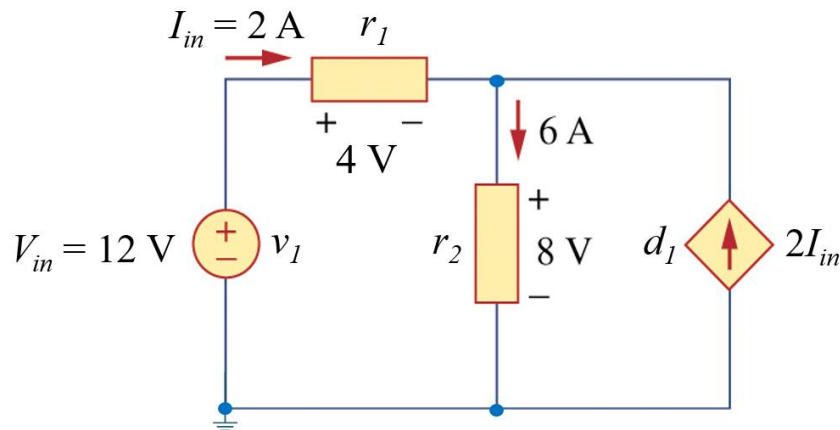
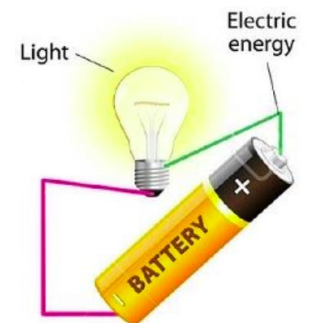
## Observations:

- The independent voltage source ( $v_1$ ) and the current-controlled current source ( $d_1$ ) are supplying power.
- The two passive elements ( $r_1$ ,  $r_2$ ) are absorbing (consuming) power.
- Note that the total power of *all* elements is equal to zero, i.e.,  $P_{v1} + P_{d1} + P_{r1} + P_{r2} = -24 - 32 + 8 + 48 = 0 \text{ W}$ .

This is *the law of conservation of energy*!



# Summary

## I. Charge and Current

- ✓ Current and electrons move in opposite direction.
- ✓ Current flows from the positive terminal to the negative terminal in a closed circuit.
- ✓ The mathematical relationship between charge and current is defined as

$$i(t) = \frac{dq(t)}{dt} \quad \text{or} \quad Q = \int_{t_0}^{t_1} i(t) dt$$

## II. Voltage

- ✓ The mathematical relationship between energy and voltage is defined as

$$v_{ab} = \frac{dw}{dq}$$

- ✓ The voltage (potential difference) between two points  $a$  and  $b$  is expressed as  $v_{ab} = v_a - v_b$ . In general,  $v_{ab} = -v_{ba}$ .

# Summary (cont'd)

## III. Power and Energy

- ✓ The mathematical relationship between power and energy is defined as

$$p(t) = \frac{dw(t)}{dt} = v(t)i(t)$$

- ✓ By convention, when the current flows from the +ve terminal to –ve terminal of an element, the element absorbs (dissipates) power. The sign of power is positive.
- ✓ Likewise, when the current flows from the –ve terminal to +ve terminal of an element, the element supplies (generates) power. The sign of power is negative.

# Summary (cont'd)

## IV. Circuit Element

- ✓ Know the difference between active element and passive element.
- ✓ Understand the meaning of ideal voltage (current) source.
- ✓ Distinguish between independent and dependent voltage (current) source.
- ✓ Be able to determine the power absorbed (or supplied) by each element.
- ✓ Remember that all closed circuits obey the law of conservation of energy.